

EE496 Computer Architecture and VHDL

Assignment 2: Crypto processor

Due date: 30 November 2018

Section 1: Combinational Logic

Task: Write a Verilog module for an N-bit adder.

N_bit_adder
<pre>`timescale 1ns / 1ps module N_bit_adder(input1,input2,answer); parameter N=32; input [N-1:0] input1,input2; output [N-1:0] answer; wire carry_out; wire [N-1:0] carry; genvar i; generate for(i=0;i<N;i=i+1) begin: generate_N_bit_Adder if(i==0) half_adder f(input1[0],input2[0],answer[0],carry[0]); else full_adder f(input1[i],input2[i],carry[i-1],answer[i],carry[i]); end assign carry_out = carry[N-1]; endgenerate endmodule // Verilog code for half adder module half_adder(x,y,s,c); input x,y; output s,c; assign s=x^y; assign c=x&y; endmodule // half adder // Verilog code for full adder module full_adder(x,y,c_in,s,c_out); input x,y,c_in; output s,c_out; assign s = (x^y) ^ c_in;</pre>

```

assign c_out = (y&c_in) | (x&y) | (x&c_in);
endmodule // full_adder

```

```


                                ts_N_bit_adder
`timescale 1ns / 1ps

module tb_N_bit_adder;
// Inputs
reg [31:0] input1;
reg [31:0] input2;
// Outputs
wire [31:0] answer;

// Instantiate the Unit Under Test (UUT)
N_bit_adder uut (
    .input1(input1),
    .input2(input2),
    .answer(answer)
);

initial begin
    // Initialize Inputs
    input1 = 1209;
    input2 = 4565;
    #100;
    // Add stimulus here
end
endmodule

```

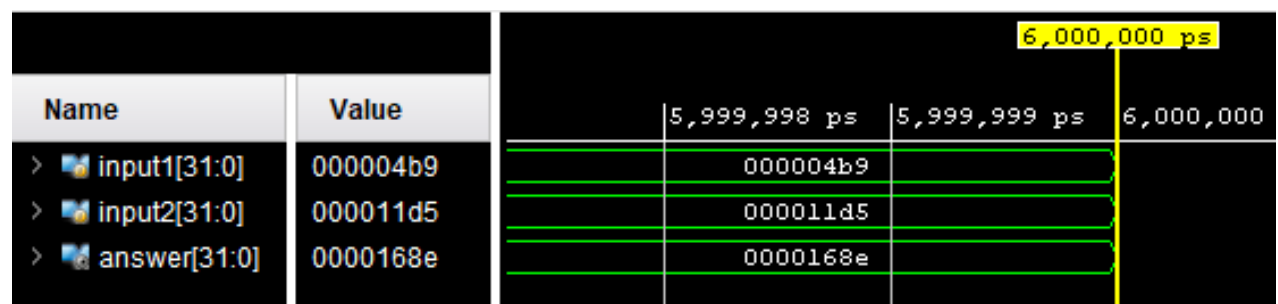Result:

Task: Implement the ALU described above in VHDL, making use of the Verilog N-bit adder that you implemented in the last section.

```

                                ALU
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity ALU is
port (
  ABUS: in std_logic_vector(15 downto 0); -- ABUS data input of the 16-bit ALU
  BBUS: in std_logic_vector(15 downto 0); -- BBUS data input of the 16-bit ALU
  ALUctrl: in std_logic_vector(3 downto 0); -- ALUctrl control input of the 16-bit ALU
  ALUOUT: out std_logic_vector(15 downto 0) -- 16-bit data output of the 16-bit ALU
);
end ALU;

```

architecture Behavioral of ALU is

-- N-bit Adder in Verilog

component N_bit_adder is

generic (

 N: integer:=32

);

port(input1: in std_logic_vector(N-1 downto 0);

 input2: in std_logic_vector(N-1 downto 0);

 answer: out std_logic_vector(N-1 downto 0)

);

end component N_bit_adder;

signal BBUS_not: std_logic_vector(16-1 downto 0);

signal tmp_out1: std_logic_vector(16-1 downto 0);

signal tmp_out2: std_logic_vector(16-1 downto 0);

signal tmp: std_logic_vector(16-1 downto 0);

begin

-- instantiate Verilog N-bit Adder in VHDL code

u1_N_bit_adder: N_bit_adder generic map (N => 16) -- ABUS + BBUS

 port map(input1 => ABUS, input2 => BBUS,answer => tmp_out1);

u2_N_bit_adder: N_bit_adder generic map (N => 16) -- ABUS + (~BBUS)

 port map(input1 => ABUS, input2 => BBUS_not,answer => tmp_out2);

u3_N_bit_adder: N_bit_adder generic map (N => 16) -- ABUS + (~BBUS) + 1 = ABUS - BBUS

 port map(input1 => tmp_out2, input2 => x"0001",answer => tmp);

BBUS_not <= not BBUS;

-- Other instructions of the 16-bit ALU in VHDL

process(ALUctrl,ABUS,BBUS,tmp_out1,tmp)

begin

case(ALUctrl) is

 when "0000" => ALUOUT <= tmp_out1; -- ADD

 when "0001" => ALUOUT <= tmp ;-- SUB

 when "0010" => ALUOUT <= ABUS and BBUS; -- AND

 when "0011" => ALUOUT <= ABUS or BBUS; -- OR

 when "0100" => ALUOUT <= ABUS xor BBUS; -- XOR

 when "0101" => ALUOUT <= not ABUS; -- NOT

 when "0110" => ALUOUT <= ABUS; -- MOVE

 when others => ALUOUT <= tmp_out1;

end case;

```
end process;

end Behavioral;
```

ts_ALU

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.all;
-- Testbench
ENTITY tb_ALU IS
END tb_ALU;

ARCHITECTURE behavior OF tb_ALU IS

    -- Component Declaration for the 16-bit ALU

    COMPONENT ALU
    PORT(
        ABUS : IN  std_logic_vector(15 downto 0);
        BBUS : IN  std_logic_vector(15 downto 0);
        ALUctrl : IN  std_logic_vector(3 downto 0);
        ALUOUT : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal ABUS : std_logic_vector(15 downto 0) := (others => '0');
    signal BBUS : std_logic_vector(15 downto 0) := (others => '0');
    signal ALUctrl : std_logic_vector(3 downto 0) := (others => '0');

    --Outputs
    signal ALUOUT : std_logic_vector(15 downto 0);

BEGIN


    -- Instantiate the 16-bit ALU
    uut: ALU PORT MAP (
        ABUS => ABUS,
        BBUS => BBUS,
        ALUctrl => ALUctrl,
        ALUOUT => ALUOUT
    );
    stim_proc: process
    begin
        ABUS <= x"000A";
```

```

BBUS <= x"0002";
ALUctrl <= x"0";
-- change ALU Control input
for i in 0 to 15 loop
  ALUctrl <= ALUctrl + x"1";
  wait for 100 ns;
end loop;
  ABUS <= x"00F6";
  BBUS <= x"000A";
  wait;
end process;

END;

```

 Result:**Task: Implement the Shifting Unit described above in VHDL.**

```


case(SHIFT_Ctrl) is
  when "1000" => SHIFTOUT <= SHIFTINPUT(3 downto 0)&SHIFTINPUT(15 downto 4);
  when "1001" => SHIFTOUT <= SHIFTINPUT(11 downto 0)&SHIFTINPUT(15 downto 12);
  when "1010" => SHIFTOUT <= SHIFTINPUT(11 downto 0) & "0000";
  when "1011" => SHIFTOUT <= "0000" & SHIFTINPUT(15 downto 4);
  when others => SHIFTOUT <= x"0000";
end case;

```

The above code for the shifter is based on the below table.

1000	ROR4	Rotate right 4 bits
1001	ROL4	Rotate left 4 bits
1010	SLL4	Shift left logic 4 bits
1011	SRL4	Shift right logic 4 bit

 Below is an image of the stimulation of the code above.




1.4 Non-Linear Lookup Operations in VHDL

To create the non-linear lookup table, the look up table entity is declared which takes in one input and returns a single output.

The table below is the input and output of the lookup table.

INPUT(Hex)	OUTPUT(hex)
00	1F
01	10
02	1D
03	17
04	1B
05	1E
06	15
07	1A
08	19
09	12
0A	1C
0B	11
0C	13
0D	14
0E	18
0F	16


Below is the result of the stimulation.

 

1.5 Structural VHD model

The structural VHDL code is made up from adding the look up table, ALU and Shifter, the result is then dependent on what the CTRL signal. The non-linear lookup table, shifter and ALU are declared as components of the structural VHDL code.

The design can be seen below.

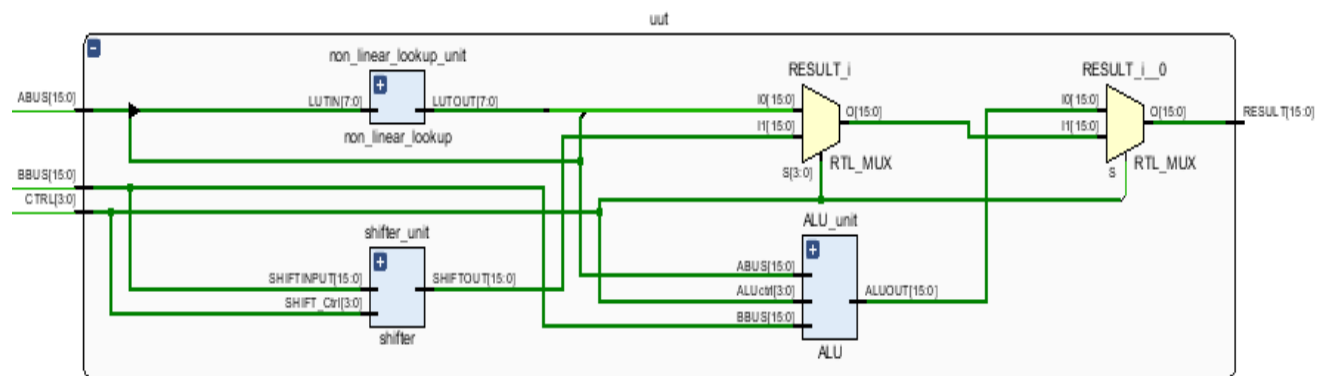

result from the lookup table will be shown and in all other cases, the result will be from the shifter.

CTRL	Component	Instruction
0000	ALU	ADD
0001	ALU	SUB
0010	ALU	AND
0011	ALU	OR
0100	ALU	XOR
0101	ALU	NOT A
0110	ALU	MOVE
0111	ALU	ADD
1000	Shifter	ROR
1001	Shifter	ROL
1010	Shifter	SLL
1011	Shifter	SRL
1100	Shifter	0
1101	Shifter	0
1110	Shifter	0
1111	Lookup	lookup

1.6 VHDL Test bench for Structural Design

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
```

```

entity Structure_tb is
end Structure_tb;

architecture Behavior of Structure_tb is

-- component declaration of structure
component Structural_model
port(
  ABUS, BBUS: in std_logic_vector(15 downto 0);
  ctrl: in std_logic_vector(3 downto 0);
  result: out std_logic_vector(15 downto 0)
);
end component;

-- inputs
signal ABUS : std_logic_vector(15 downto 0) := (others => '0');
signal BBUS : std_logic_vector(15 downto 0) := (others => '0');
signal ctrl : std_logic_vector(3 downto 0) := (others => '0');

-- output
signal result : std_logic_vector(15 downto 0);

begin

-- initiate structural model
uut: structural_model port map(
  ABUS => ABUS,
  BBUS => BBUS,
  ctrl => ctrl,
  result => result
);

stim_proc: process
  begin
    ABUS <= x"0001";
    BBUS <= x"0002";

    ctrl <= x"0";

    wait for 10ns;
    if result = x"0003" then
      report"PASS: 1";
    else
      report"FAIL: 1";
    end if;

    ctrl <= x"1";
  end process;

```



```
wait for 10ns;
if result = x"FFFF" then
    report"PASS: 2";
else
    report"FAIL: 2";
end if;

ctrl <= x"2";
wait for 10ns;
if result = x"0000" then
    report"PASS: 3";
else
    report"FAIL: 3";
end if;

ctrl <= x"3";
wait for 10ns;
if result = x"0003" then
    report"PASS: 4";
else
    report"FAIL: 4";
end if;

ctrl <= x"4";
wait for 10ns;
if result = x"0003" then
    report"PASS: 5";
else
    report"FAIL: 5";
end if;

ctrl <= x"5";
wait for 10ns;
if result = x"FFFE" then
    report"PASS: 6";
else
    report"FAIL: 6";
end if;

ctrl <= x"6";
wait for 10ns;
if result = x"0001" then
    report"PASS: 7";
else
    report"FAIL: 7";
```

```
end if;

ctrl <= x"7";
wait for 10ns;
if result = x"0003" then
    report"PASS: 8";
else
    report"FAIL: 8";
end if;

ctrl <= x"8";
wait for 10ns;
if result = x"2000" then
    report"PASS: 9";
else
    report"FAIL: 9";
end if;

ctrl <= x"9";
wait for 10ns;
if result = x"0020" then
    report"PASS: 10";
else
    report"FAIL: 10";
end if;

ctrl <= x"a";
wait for 10ns;
if result = x"0020" then
    report "PASS: 11";
else
    report "FAIL: 11";
end if;

ctrl <= x"b";
wait for 10ns;
if result = x"0000" then
    report "PASS: 12";
else
    report "FAIL: 12";
end if;

ctrl <= x"c";
wait for 10ns;
if result = x"0" then
    report "PASS: 13";
else
```

```

    report "FAIL: 13";
end if;

ctrl <= x"d";
wait for 10ns;
if result = x"0" then
    report "PASS: 14";
else
    report "FAIL: 14";
end if;

ctrl <= x"e";
wait for 10ns;
if result = x"0" then
    report "PASS: 15";
else
    report "FAIL: 15";
end if;


ctrl <= x"f";
wait for 10ns;
if result = x"10" then
    report "PASS: 16";
else
    report "FAIL: 16";
end if;

end process;

end;

```

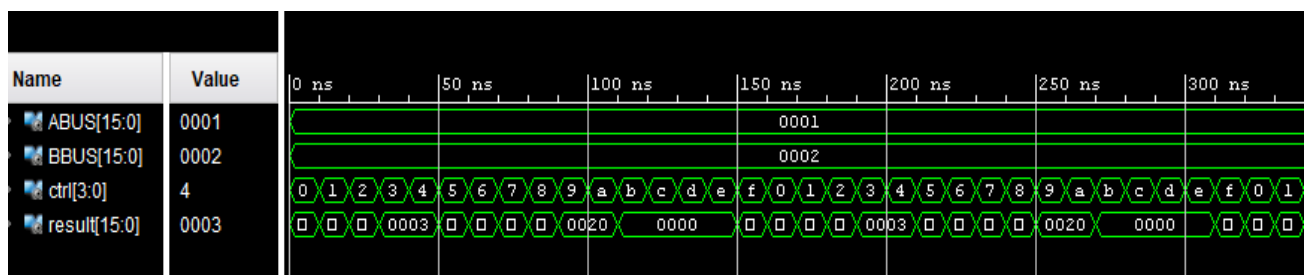Above is the test bench that was used to test all 12 possible modes of operation as can be seen when the A and B were set to 1, and 2 respectively the result will be as follows.



2.1 Registers

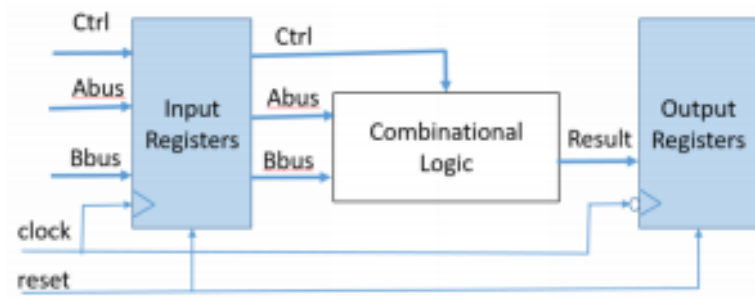


Figure 6 Synchronous system

From the image above to create a synchronous system there needs to be an input and output registered the image above also includes what inputs are needed.

If the clock edge is rising and reset is disabled, the combinational logic system reads in the input values as seen below.

```
process(clock,reset)
begin
if rising_edge(clock) then
  if reset = '1' then
    ctrl <= "0000";
    ABUS <= x"0000";
    BBUS <= x"0000";
  else
    ctrl <= ctrlin;
    ABUS <= ABUSin;
    BBUS <= BBUSin;
  end if;
end if;
end process;
```

If the clock edge is falling and reset is disabled, then the combinational logic system is writing out the result.

```
process(clock,reset)
begin
if falling_edge(clock) then
  if reset = '1' then
    result <= x"0000";
  else
    result <= resultin;
  end if;
end if;
end process;
```

2.2 Memory



Figure 7 Register file

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity register_file is
  Port (
    Abus : out std_logic_vector(15 downto 0); --srca
    Bbus : out std_logic_vector(15 downto 0); --srcb
    result : in std_logic_vector(15 downto 0); --res
    writeEnable : in std_logic; --rdwen
    regAsel : in std_logic_vector(3 downto 0); --ra
    regBsel : in std_logic_vector(3 downto 0); --rb
    writeRegSel : in std_logic_vector(3 downto 0); --rd
    reset : in std_logic;
    clock : in std_logic
  );
end register_file;

architecture Behavioral of register_file is

  type memory is array(0 to 15) of std_logic_vector(15 downto 0);
  signal REG_FILE: memory :=(
    0 => x"0001",
    1 => x"c505",
    2 => x"3c07",
    3 => x"d405",
    4 => x"1186",
    5 => x"f407",
    6 => x"1086",
    7 => x"4706",
    8 => x"6808",
    9 => x"baa0",
    10 => x"c902",
    11 => x"100b",
    12 => x"c000",
    13 => x"c902",

```

```

14 => x"100b",
15 => x"B000",
others => (others => '0')
);

begin

write_op: process(clock)
begin
if(falling_edge(clock)) then
    if(writeEnable='1') then
        REG_FILE(to_integer(unsigned(writeRegSel))) <= result;
    end if;
end if;
end process;

read_op: process(clock)
begin
if(rising_edge(clock)) then
    if(reset='1') then
        ABUS <= x"0000";
        BBUS <= x"0000";
    else
        ABUS <= REG_FILE(to_integer(unsigned(regAsel)));
        BBUS <= REG_FILE(to_integer(unsigned(regBsel)));
    end if;
end if;
end process;

end Behavioral;

```

2.3 Complete Crypto Coprocessor

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity coprocessor is
    Port (
        clock: in std_logic;
        reset: in std_logic;
        ctrl: in std_logic_vector (3 downto 0);
        regA : in std_logic_vector(3 downto 0); --ra
        regB : in std_logic_vector(3 downto 0); --rb
        writeReg : in std_logic_vector(3 downto 0)
    );
end coprocessor;

```

architecture Behavioral of coprocessor is

```
--register file
component register_file is
port(
  Abus : out std_logic_vector(15 downto 0); --srca
  Bbus : out std_logic_vector(15 downto 0); --srcb
  result : in std_logic_vector(15 downto 0); --res
  writeEnable : in std_logic; --rdwrite_enable
  regAsel : in std_logic_vector(3 downto 0); --ra
  regBsel : in std_logic_vector(3 downto 0); --rb
  writeRegSel : in std_logic_vector(3 downto 0); --rd
  reset : in std_logic;
  clock : in std_logic
);
end component register_file;

--structural component
component structural_model is
port(
  ABUS: in std_logic_vector(15 downto 0);
  BBUS: in std_logic_vector(15 downto 0);
  CTRL: in std_logic_vector(3 downto 0);
  RESULT: out std_logic_vector(15 downto 0)
);
end component structural_model;

-- internal signals
signal write_enable: std_logic;
signal read1, read2, write : std_logic_vector(15 downto 0);
signal tmp1, tmp2: std_logic_vector(3 downto 0);

begin
  uut1: register_file port map(
    clock=> clock,
    reset => reset,
    writeEnable => write_enable,
    result => write,
    regAsel => regA,
    regBsel => regB,
    writeRegSel => tmp2,
    Abus => read1,
    Bbus => read2
  );

  uut2: Structural_model port map(
    ABUS => read1,
    BBUS => read2,
    ctrl => tmp1,
    result => write
```

```
);

process(clock,reset) begin
if(rising_edge(clock)) then
    if (reset ='1') then
        tmp1 <= x"0";
        tmp2 <= x"0";
    else
        tmp1 <= ctrl;
        tmp2 <= writeReg;
        if (tmp1 = "0111") then
            write_enable <= '0';
        else
            write_enable <= '1';
        end if;
    end if;
end if;
end process;

end Behavioral;
```

2.4 Test Program

A stimulus generator is created that implements the code specified in the task after performing a system reset.

